



Green University of Bangladesh

Department of Computer Science and Engineering

CT-02


Course Title: Introduction to Electrical Engineering

Course code: EEE 201

Date of Submission: 21.12.2020

Submitted to:	Submitted by :
Name : Md. Tariqul Islam	Name : Jakirul Islam
Designation : Lecturer	ID : 193002101
Department : EEE	Department : CSE
Green university of Bangladesh	Green university of bangladesh

Ans to the Q. no: 1

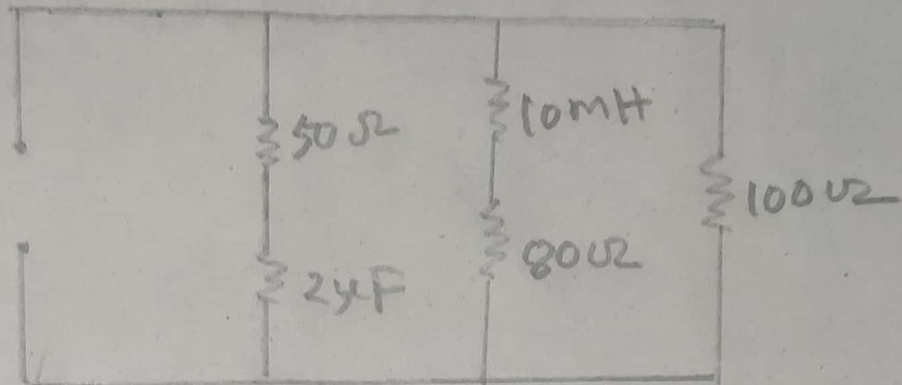

$$Z_1 = 50 + \frac{1}{j\omega C}$$

$$= 50 + \frac{-j}{(2\pi)(2 \times 10^3)(2 \times 10^{-6})}$$

$$Z_1 = 50 - j39.79$$

$$Z_2 = 80 + j\omega L$$

$$= 80 + j(2\pi)(2 \times 10^3)(10 \times 10^{-3})$$

$$= 80 + j125.66$$

$$Z_3 = 100$$

now,

$$\frac{1}{Z} = \frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3}$$

$$\frac{1}{Z} = \frac{1}{100} + \frac{1}{50 - j39.79} + \frac{1}{80 + j125.66}$$

$$\frac{1}{Z} = 10^{-3} (10 + 12.24 + j9.745 + 3.605 - j5.663)$$


$$= (25.85 + j4.082) \times 10^{-3}$$

$$= 26.17 \times 10^{-3} \angle 8.97^\circ$$

$$\therefore Z = 38.21 \angle -8.97^\circ \Omega$$

Ans.

Ans to the Q. no: 2

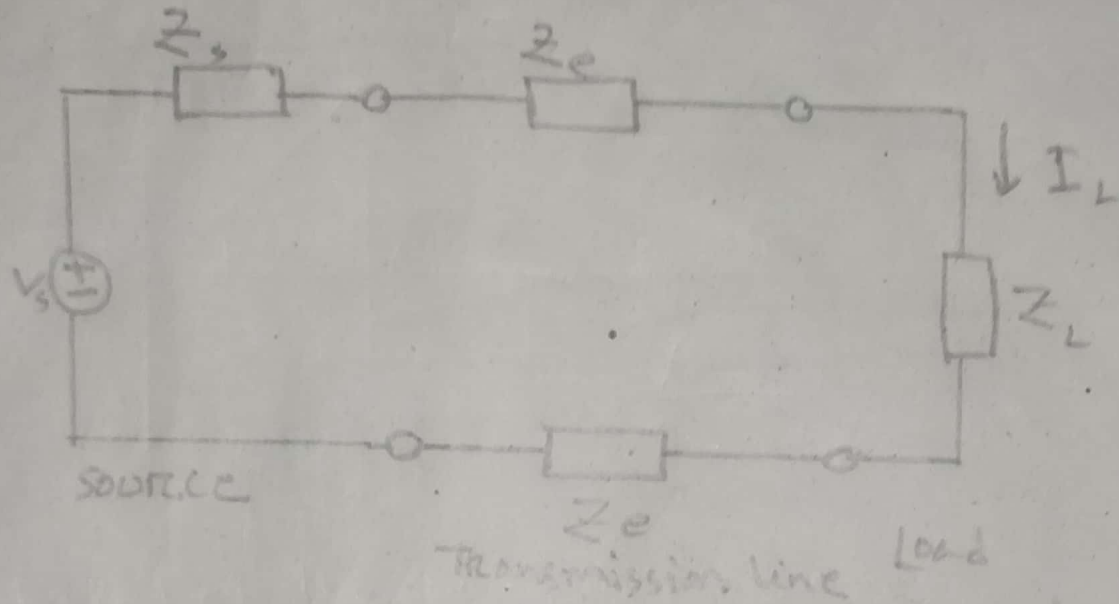

Given that,

$V_s = 1150 \text{ V}$, source impedance

$Z_s = 1 + j0.5$, line impedance

$Z_e = 0.4 + j0.3$, and load impedance

$Z_L = 23.2 + j18.9$, find the load current I_L

We know,

$$Z = Z_s + 2Z_e + Z_L$$

$$Z = (1 + 0.8 + 23.2) + j(0.5 + 0.6 + 18.9)$$

$$Z = 25 + j20$$

we know,


$$I_L = \frac{V_s}{Z}$$

$$= \frac{1150^\circ}{32.02 \angle 38.66^\circ}$$

$$I_L = 3.592 \angle -38.66^\circ \text{ A}$$

Ans.

Ans to the q.no: 3

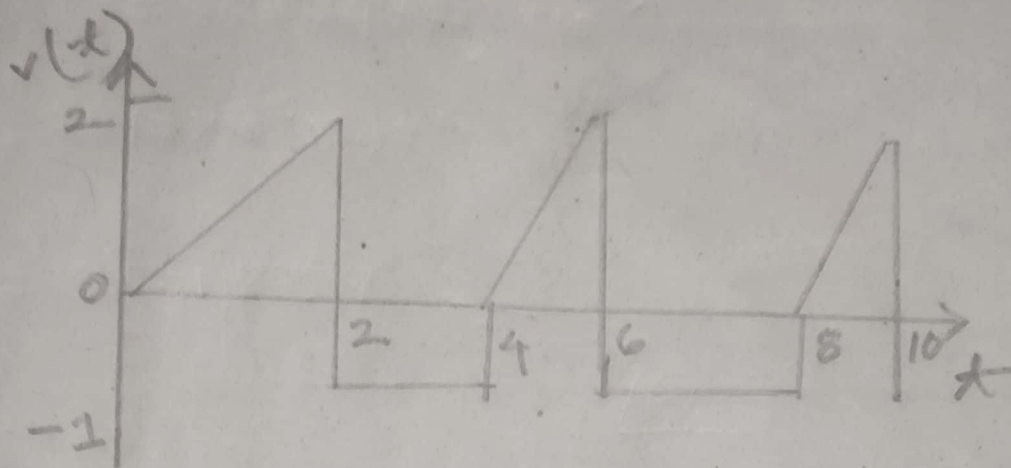

the period of the waveform is $T = 4$

now,

$$v(t) = \begin{cases} t, & 0 < t < 2 \\ -t, & 2 < t < 4 \end{cases}$$

the RMS

$$I_{rms} = \sqrt{\frac{1}{T} \int_0^T v^2 dt}$$

$$= \sqrt{\frac{1}{4} \int_0^4 v^2 dt}$$

$$= \sqrt{\frac{1}{4} \left[\int_0^2 (t)^2 dt + \int_2^4 (-t)^2 dt \right]}$$

$$= \frac{1}{4} \left[1 \cdot \frac{x^3}{3} \right]$$

$$= \sqrt{\frac{1}{4} \left[1 \left(\frac{8}{3} - 0 \right) + (1 \times 4 - 1 \times 2) \right]}$$

$$= \sqrt{\frac{1}{4} \left(\frac{8}{3} + 2 \right)}$$

$$= \sqrt{\frac{14}{12}}$$

$$= 1.080 \text{ A}$$

Ans.