



Final Assignment

Course Title: Introduction to Electrical Engineering Lab

Course Code: EEE 202

Submitted Date:18-01-2021

Submitted To :	Submitted By
Name : Md. Tariqul Islam	Name : Jakirul Islam
Designation : Lecturer	Id : 193002101
Department of EEE	Section : DC
Green University of Bangladesh	Department of CSE
	Green University of Bangladesh

Ans to the Q.no:1

a) we know,

$$\begin{aligned}\text{Complex power, } S &= V_{\text{rms}} \times I_{\text{rms}}^* \\ &= (110 \angle 85^\circ) \times (0.4 \angle -15^\circ) \\ &= 15.05 + j41.35 \text{ VAR} \\ &= 44 \angle 70^\circ \text{ VA}\end{aligned}$$

Here,

$$V_{\text{rms}} = 110 \angle 85^\circ \text{ V}$$

$$I_{\text{rms}} = 0.4 \angle 15^\circ \text{ A}$$

Ans.

b) Apparent power,
44 VA

c) Real power = 15.05 W

Reactive power = 41.35 VAR

c) Power factor,

$$\begin{aligned}PF &= \cos(\theta) \\ &= \cos(70) = 0.34\end{aligned}$$

and;


$$\text{load impedance, } Z = \frac{V_{\text{rms}}}{I_{\text{rms}}} = \frac{110 \angle 85^\circ}{0.4 \angle 15^\circ} = 94.05 + j28.4 \Omega$$

Ans: a) $44 \angle 70^\circ \text{ VA}$, 44 VA

b) 15.05 W , 41.35 VAR

c) 0.342 lagging, $94.06 + j258.4 \Omega$

Ans to the Q.no:2

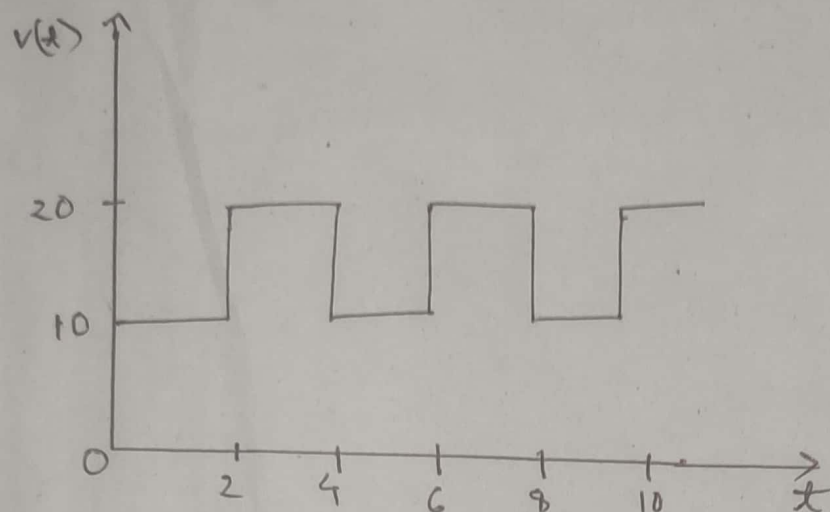

Time Period, $T = 4$

$$v(t) = \begin{cases} 10, & 0 \leq t < 2 \\ 20, & 2 \leq t < 4 \end{cases}$$

We know,

$$V_{rms}^2 = \frac{1}{T} \int_0^T v^2(t) dt$$

Now,

$$V_{rms}^2 = \frac{1}{4} \int_0^2 (10)^2 dt + \int_2^4 (20)^2 dt$$

$$V_{rms}^2 = \frac{1}{4} [200 + 800]$$

$$V_{rms}^2 = \frac{1}{4} [1000]$$


$$V_{rms} = 250$$

$$\therefore V_{rms} = 15.81 \text{ V}$$

Ans: 15.81 V

5

Ans to the Q.no: 3

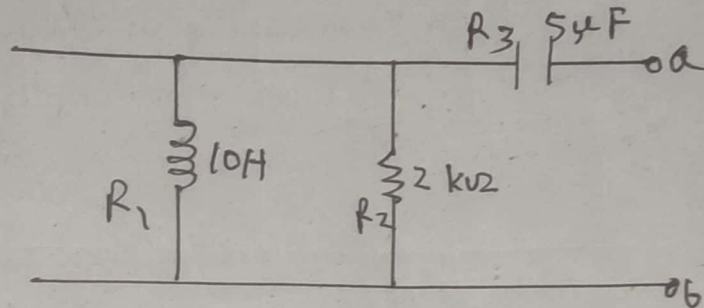

Calculating Z_n , the current source as open circuit,

$$10H = j \times 200 \times 10 \\ = j2000 \Omega$$

$$5\mu F = \frac{1}{j \times 200 \times 5 \times 10^{-6}} \\ = -j1000 \Omega$$

Here,

$$I = 4 \cos(200t + 30^\circ) A \\ = 4 \angle 30^\circ A$$

$$\omega = 200$$


R_1 and R_2 Parallel

$$\therefore Z_1 = \frac{j2000 \times 2000}{j2000 + 2000} \\ = 1000 + j1000 \Omega$$

and, Z_1 and R_3 are series,

$$Z_{th} = (1000 + j1000 - j1000) \Omega \\ = 1000 \Omega$$

calculating I_N ,

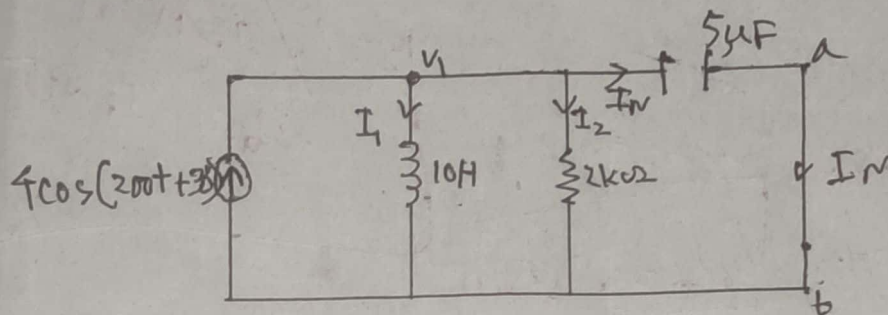

using nodal Analysis,

$$4\angle 30^\circ = I_1 + I_2 + I_N$$

$$4\angle 30^\circ = \frac{v_1 - 0}{j2000} + \frac{v_1 - 0}{2000} + \frac{v_1 - 0}{-j1000}$$

$$4\angle 30^\circ = -j5 \times 10^{-4} v_1 + 5 \times 10^{-4} v_1 + j1 \times 10^{-3} v_1$$


$$\therefore v_1 = 1892.82 - j1678.46 \text{ V}$$

$$\therefore I_N = \frac{1892.82 - j1678.46}{-j1000}$$

$$= 1.678 + j1.89 \text{ A}$$

Ans.

Ans to the Q.no: 4

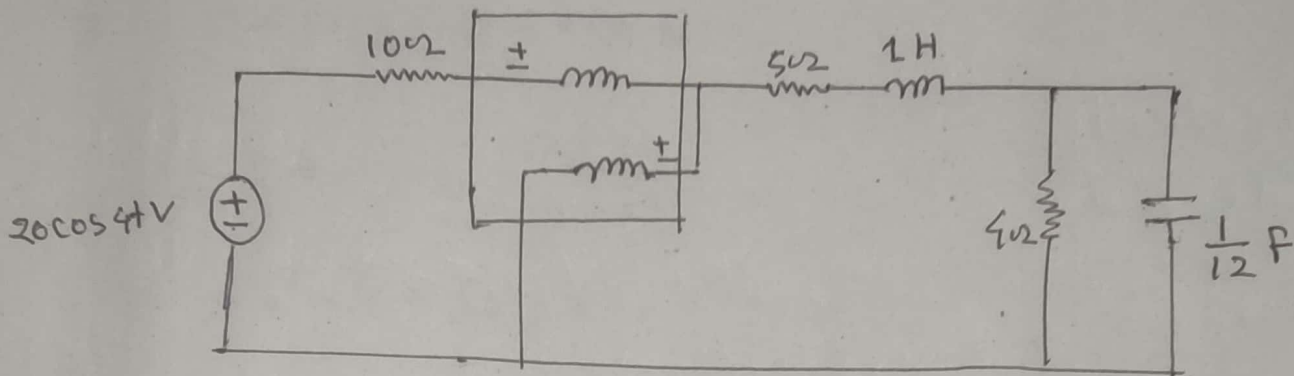

The wattmeter reads the power absorbed by the element to its right side.


$$W = 4$$

$$20\cos(4t) \rightarrow 20\angle 0^\circ$$

$$1\text{ H} \rightarrow j\omega L = j \times 4 \times 1 = j4$$

$$\frac{1}{12}\text{ F} \rightarrow \frac{1}{j\omega C} = \frac{1}{j \times 4 \times \frac{1}{12}} = -j3$$

Consider the following circuit.

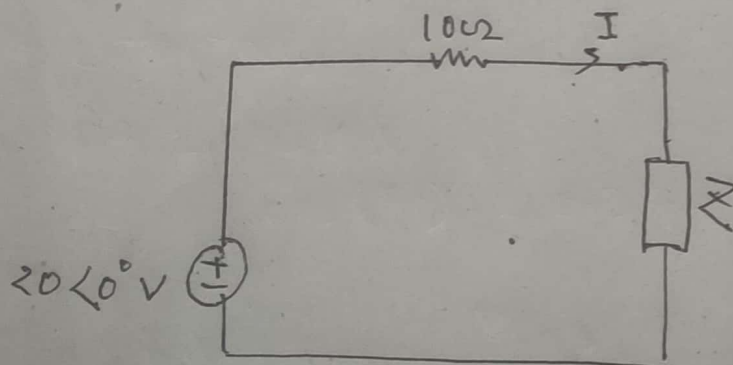

Now,

$$Z = 5 + j4 + 4 \parallel -j3$$

$$= 5 + j4 + \frac{4 \times (-j3)}{4 - j3}$$

$$\therefore Z = 6.44 + j2.08$$

$$I = \frac{20}{6.44 + j2.08}$$

$$= 1.207 \angle -7.21^\circ$$

\therefore Complex power,

$$S = \frac{1}{2} |I|^2 Z$$


$$= \frac{1}{2} \cdot (1.207)^2 \cdot (6.44 + j2.08)$$

$$= 4.691 \text{ W}$$

Ans.

9

Ans to the Q.no:5

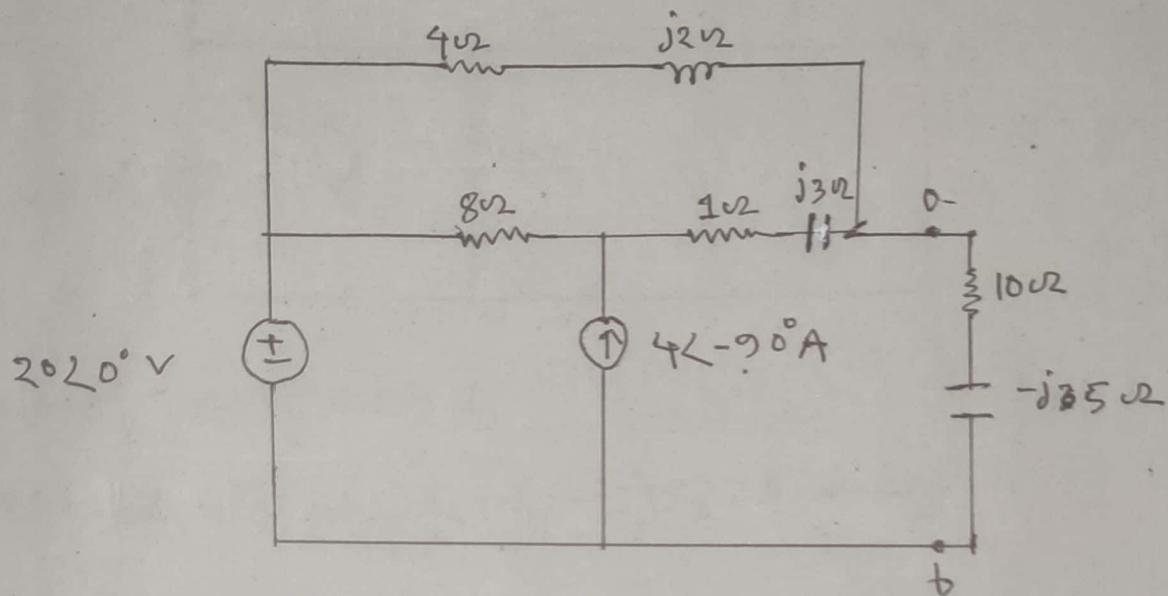

now,

voltage source short circuit and current source open circuit.


$$Z_n = Z_{th} = (4 + j2) \parallel (3 + 1 - j3)$$

$$= \frac{(4 + j2) \times (9 - j3)}{(4 + j2) + (9 - j3)}$$

$$\therefore Z_n = 3.1764 + j0.7058 \Omega$$

Again, ~~now~~

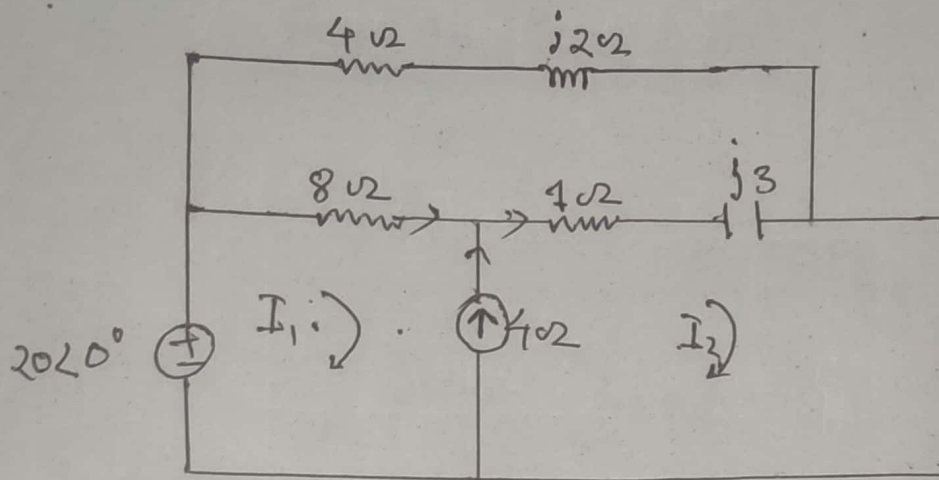short circuit terminal ab. Solve I_n using mesh Analysis.



Calculate super mesh 1,

$$20 + 8I_1 + (1 - j3)I_2 - (9 - j3)I_3 = 0 \quad \text{--- (I)}$$

mesh 2 calculate KCL

$$I_1 = I_2 + 4 \quad \text{--- (II)}$$

now, mesh 3 calculate,


$$-8I_1 - (1 - j3)I_2 = 0 \quad \text{--- (III)}$$

$$\begin{aligned} \therefore I_1 = I_2 &= \frac{50 - j62}{9 - j3} \\ &= \frac{79.65 \angle -51.11^\circ}{9.487 \angle -18.43^\circ} \\ &= 8.396 \angle -32.68^\circ \text{ A} \end{aligned}$$


Norton equivalent, find I_0

$$\begin{aligned} I_0 &= \frac{Z_n}{Z_n + 10 - j5} \times I_{sc} \\ &= \frac{3.1764 + j0.7058}{3.1764 + j0.7058 + 10 - j5} \times (8.396 \angle -32.68^\circ) \\ &= 1.971 \angle -2.101^\circ \text{ A} \quad \text{Ans} \end{aligned}$$

Ans to the Q.no: 6

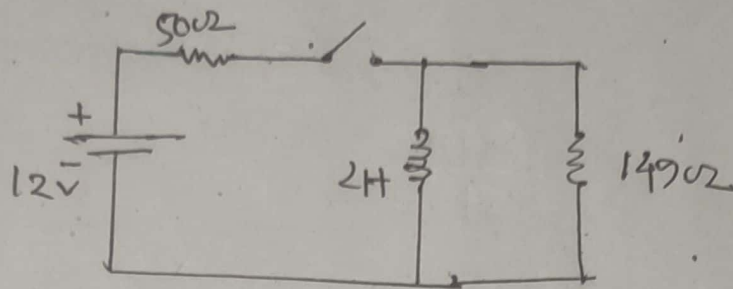

In DC circuit Inductance is $= 0$

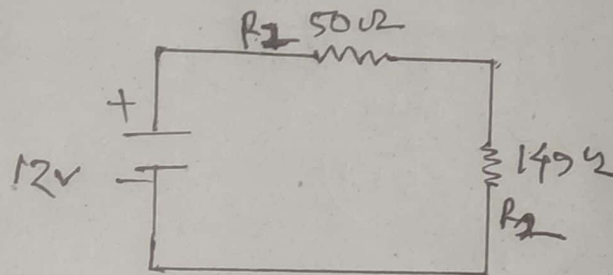

we can see

$R = R_1 + R_2$ is in series

$$\therefore R = 50 + 149\Omega$$
$$= 199\Omega$$

we know,

$$V = IR$$

$$I = \frac{V}{R} = \frac{12}{199} \text{ A}$$

$$\therefore I = 0.06 \text{ A}$$

voltage across $R_2 = V_2$

$$V_2 = \frac{I}{R_2}$$

$$= \frac{0.06 \text{ A}}{149}$$

$$= 0.0004 \text{ V}$$

And,

$$\text{current, } I_2 = \frac{V_2}{R_2}$$

$$= \frac{0.0004}{149}$$

$$= 2.68 \times 10^{-6} \text{ A}$$



∴ total current is $= 0.06 \text{ A}$

current following ~~through~~ through the ~~source~~ $= 2.68 \times 10^{-6} \text{ A}$

Ans,