

# Electrical & Electronics Engineering

## EEE Lab Report

Course: Electronic Devices and Circuits & Pulse Techniques Lab

Course Code: EEE 204

Experiment No: 07

Experiment Name: Differentiator

Date of Performance: 15/04/2021

Date of Submission: 21/04/2021

Submitted By: Md. Omor Faruk Id No: 192002006 Section: 192 DB Department of Computer Science & Engineering Green University of Bangladesh	Submitted To: Mr. Sharif Nafis Mahmood Lecturer Department of EEE Green University of Bangladesh
--	--

---

**Signature and Date**

**Mr. Md. Sharif Nafis Mahmood**

**Lecturer**

**Department of EEE**

**Green University of Bangladesh**

Experiment No: 07

Experiment Name: Differentiator

Aim: To design and setup a Differentiator circuit using OP AMP 741C and Plot their Pulse response.

Objectives: After completion of this experiment, we will be able to design and setup a differentiator circuit using OP AMP.



Equipments/Components:

Sl. No.	Name and Specification	Quantity required
01.	Dual power supply $\pm 15V$	1
02.	Function generator (0-1MHz)	1
03.	Oscilloscope	1
04.	Bread board	1
05.	IC 741C	1
06.	Resistor	1
07.	Capacitor	1
08.	Probes and connecting wires	As required

Principle: It is an OP AMP circuit which performs the mathematical operation of differentiation. That is the output waveform is the derivative or differential of the input voltage. That is

$$V_o = -R_f C \frac{d(V_{in})}{dt}$$

The differentiator circuit is constructed from basic inverting

amplifier by replacing the input resistance  $R_i$  with capacitor  $C$ . This circuit also works as high pass filter.

### Procedure:

01. Check the components.
02. Setup the circuit on the breadboard and check the connections.
03. Switch on the power supply.
04. Keep the oscilloscope in AC coupling mode.
05. Give  $V_i = 2V_{pp}$ , 1KHz square wave.
06. Observe input and output on two channels of the oscilloscope simultaneously.
07. Note down and draw the input and output waveforms on the graph.



# Circuit Diagram:

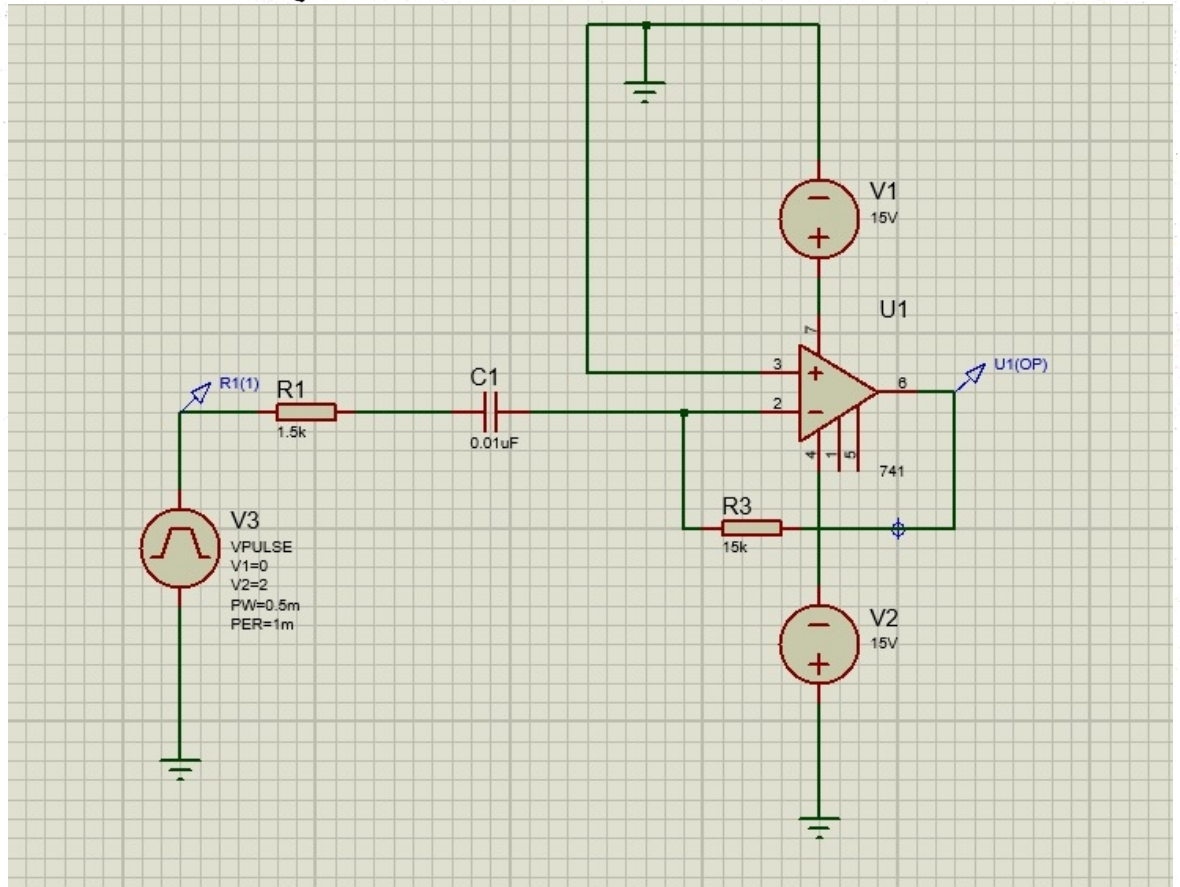


Figure: Differntiator(Proteus)

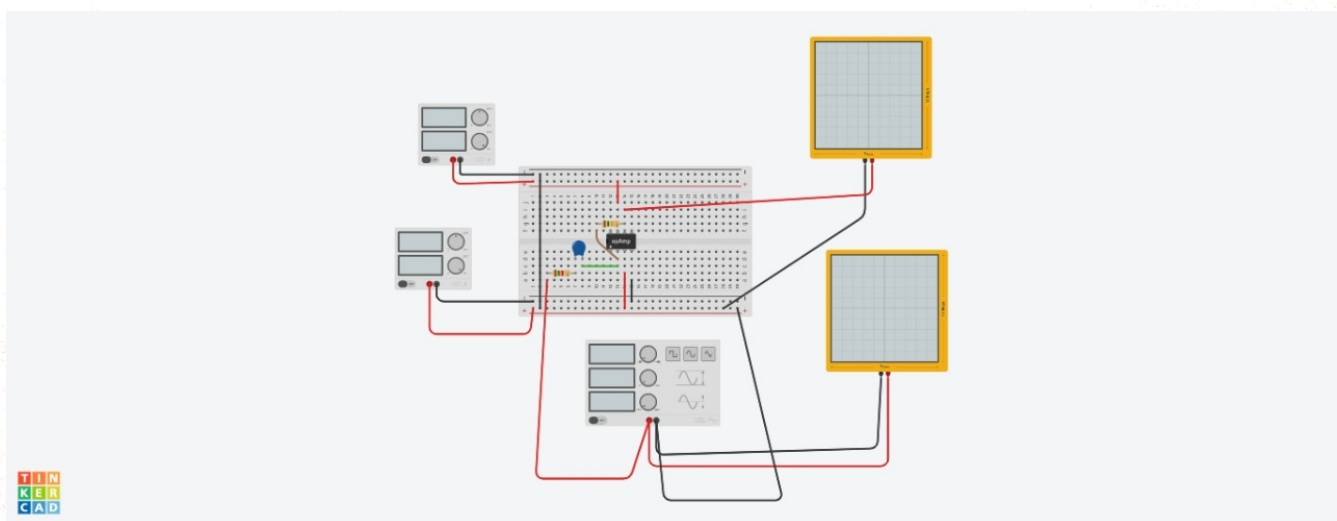


Figure: Differentiator(TinkerCAD)

Discussion:

Differentiator amplifier is an op-amp circuit configuration - which is inverse of the integrator circuit. It produces an output signal - where the instantaneous amplitude is proportional to the rate of change of the applied input voltage.

Mathematically speaking, the output signal of a Differentiator is the first order derivative of the input signal.

From this experiment, - we - will be able to design an op-amp circuit configuration - which - will produce a first order derivative signal as an output signal of the input signal.

Finally we can say that, this experiment



is more effective to gain knowledge a differentiator amplifier and from this experiment - we can realize that, how a differentiator amplifier - works by a graph clearly. So at last we can say that, this experiment is more important for us.

### References:

- [1] Lab Manual for EEE 204 Course  
[Made & Edited by Mr. Md. Sharif  
Nafis Mahmood, Lecturer, Dept. of  
EEE, Green University of  
Bangladesh]
- [2] <https://www.electronicshub.org/operational-amplifier-as-differentiator/>