



GREEN UNIVERSITY OF BANGLADESH



Department of Computer Science & Engineering

Group Assignment (Odd)

Course Code: EEE-203

Course Title: Electronic Devices and Circuits & Pulse Techniques

Date of Submission : 30.04.2021

Submitted to:

Name : Md. Shariful Islam

Designation : Lecture

Dept : EEE

Green University Of Bangladesh

Submitted by:

Name : Jakirul Islam

ID : 193002101

Section : 193(DC)

Dept. : CSE

Remark

Ans to the Q.no: 1

Given that,

$$V_o = -10V_1 + 5 \frac{dV_2}{dt} + 2 \int V_3 dt$$

$$\Rightarrow V_o = -(10V_1 + 5 \frac{dV_2}{dt} - 2 \int V_3 dt)$$

for V_1 ,

$$V_o = 10V_1$$

$$\therefore \text{let, } R_f = 10 \times 1 \Omega$$

$$R_i = 1 \Omega$$

for V_2 ,

$$V_o = -5 \frac{dV_2}{dt}$$

$$\therefore \text{let, } R = 5 \Omega$$


$$C = 0.7246 F$$

for V_3 ,

$$V_o = -2 \int V_3 dt$$

$$\therefore \text{let, } R = 2 \Omega$$

$$C = 0.7246 F$$

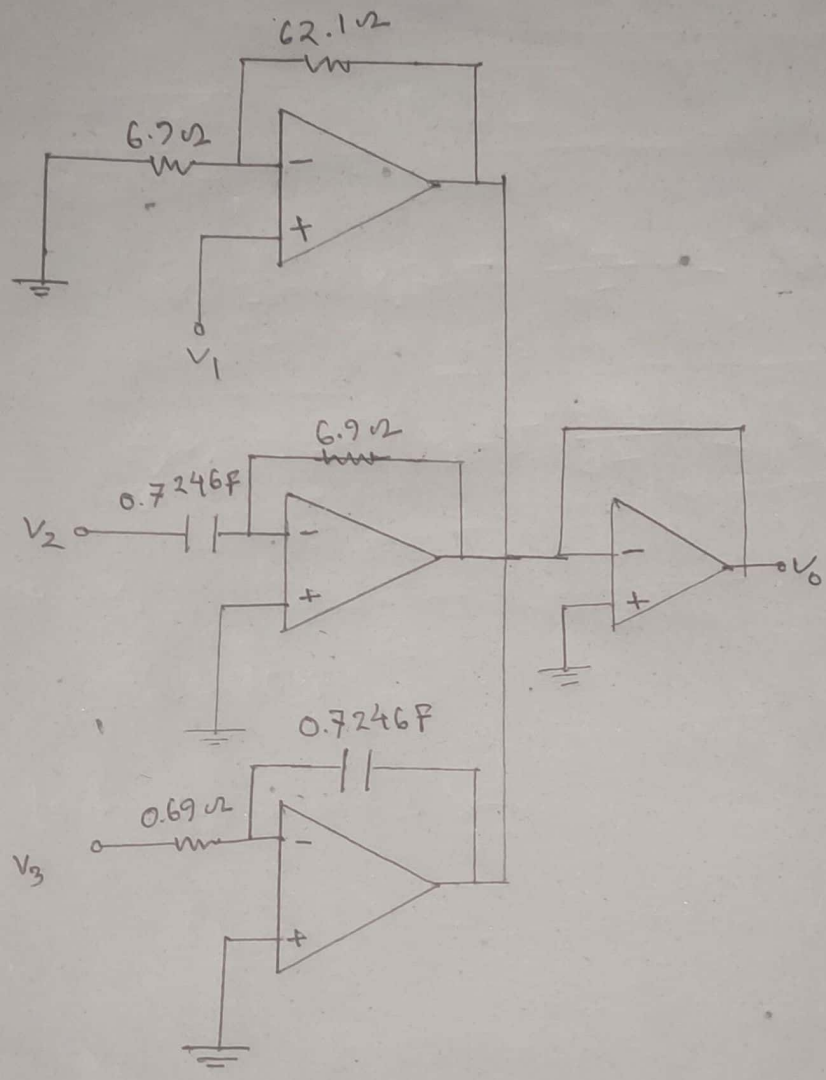

Ans to the Q.no: 2

Given that,

$$V_0 = 5V_1 - 10 \frac{dV_2}{dt} + 2 \int V_3 dt$$

$$\Rightarrow V_0 = -(-5V_1 + 10 \frac{dV_2}{dt} - 2 \int V_3 dt)$$

For, V_1 ,

$$V_0 = -5V_1$$

$$\therefore \text{let, } R_f = 34.5 \Omega$$

$$R_i = 6.9 \Omega$$

For, V_2 ,

$$V_0 = 10 \frac{dV_2}{dt}$$

$$\therefore \text{let, } R = 6.9 \Omega$$


$$C = 1.449 F$$

For, V_3 ,

$$V_0 = -2 \int V_3 dt$$

$$\therefore \text{let, } R = 0.69 \Omega$$

$$C = 0.7246 F$$

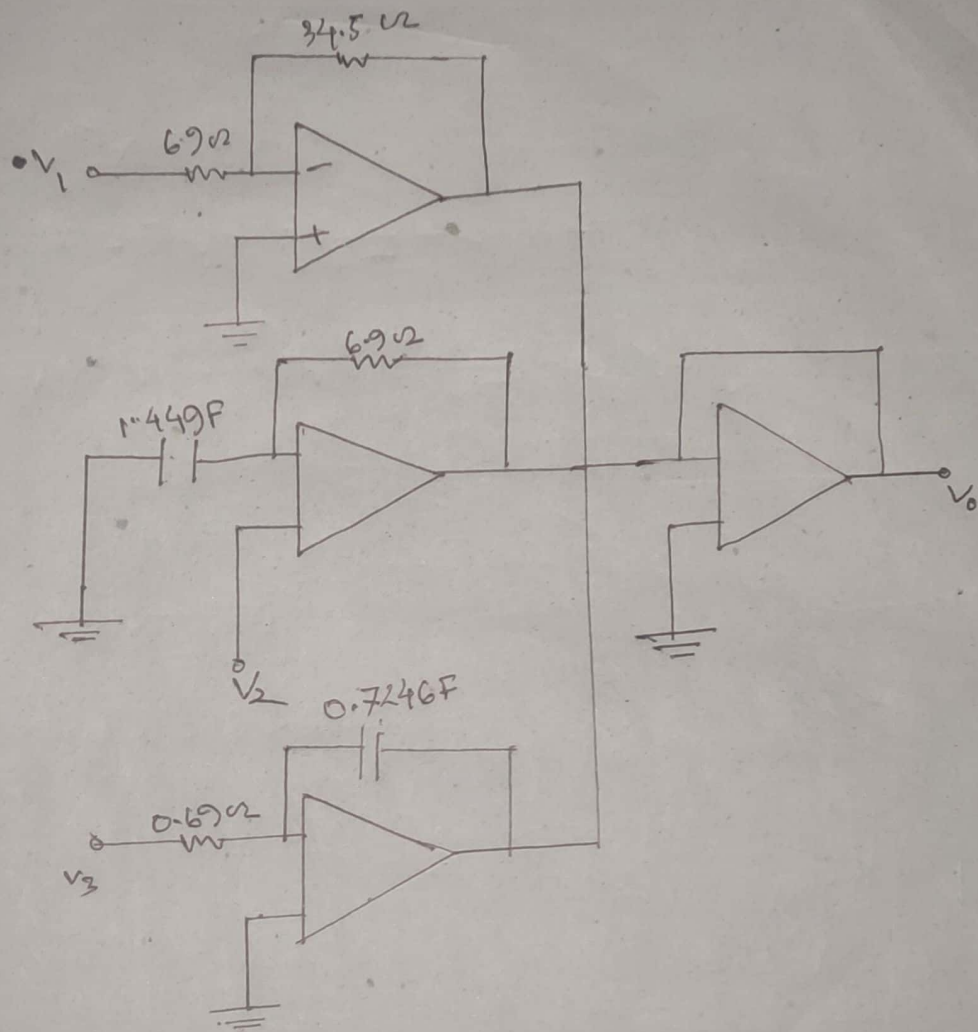

5

Ans to the Q.no: 3

Given that,

$$V_o = - \int (v_1 + 4v_2 + 10v_3) dt$$

$$\Rightarrow V_o = \int (-v_1 - 4v_2 - 10v_3) dt$$

For v_1 ,

$$V_o = - \int v_1 dt$$

$$\therefore \text{let, } R = 6.9 \Omega$$

$$C = 0.1449 F$$

$$\text{For } v_2, V_o = - \int 4v_2 dt$$


$$\therefore \text{let, } R = 6.9 \Omega$$

$$C = 0.0362 F$$

$$\text{For } v_3, V_o = -10 \int v_3 dt$$

$$\text{let, } R = 6.9 \Omega$$

$$C = 0.0144 F$$

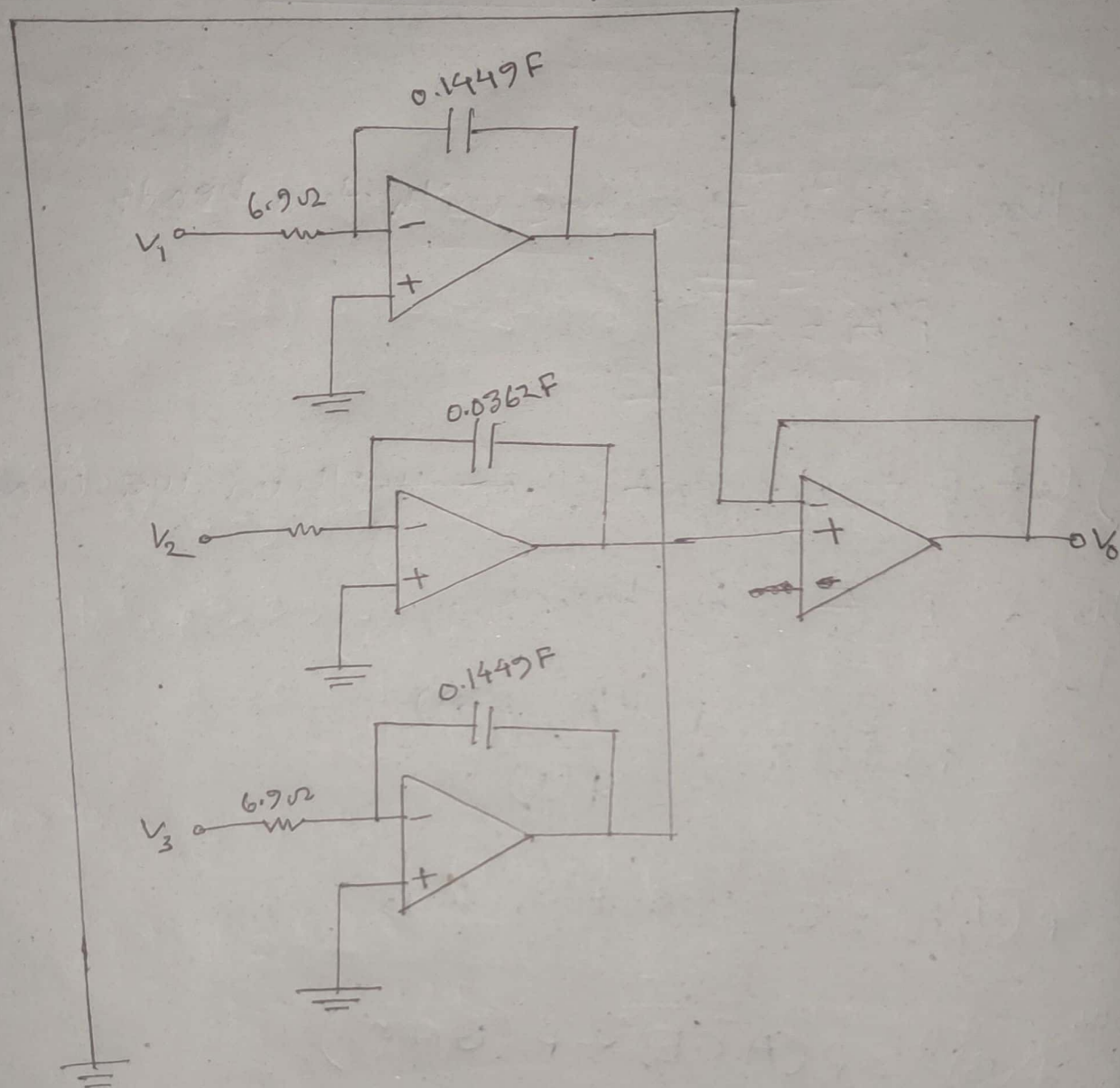

Ans to the Q.no: 4

Given that,

$$R = 50 \text{ k}\Omega = 50 \times 10^3 \Omega$$

$$C = 10 \mu\text{F} = 1 \times 10^{-5} \text{ F}$$

$$\frac{dv_i(t)}{dt} = \begin{cases} 20 \text{ V s}^{-1} & 0 \leq t < 5 \text{ ms} \\ -10 \text{ V s}^{-1} & 5 \leq t < 15 \text{ ms} \end{cases}$$

For

$$\frac{dv_i(t)}{dt} = 20 \text{ V s}^{-1}$$


$$v_o(t) = -50 \times 10^3 \times 1 \times 10^{-5} \times 20 \\ = -10 \text{ V}$$

For

$$\frac{dv_i(t)}{dt} = -10 \text{ V s}^{-1}$$

$$v_o(t) = -50 \times 10^3 \times 1 \times 10^{-5} \times (-10) \\ = 5 \text{ V}$$

Waveform:

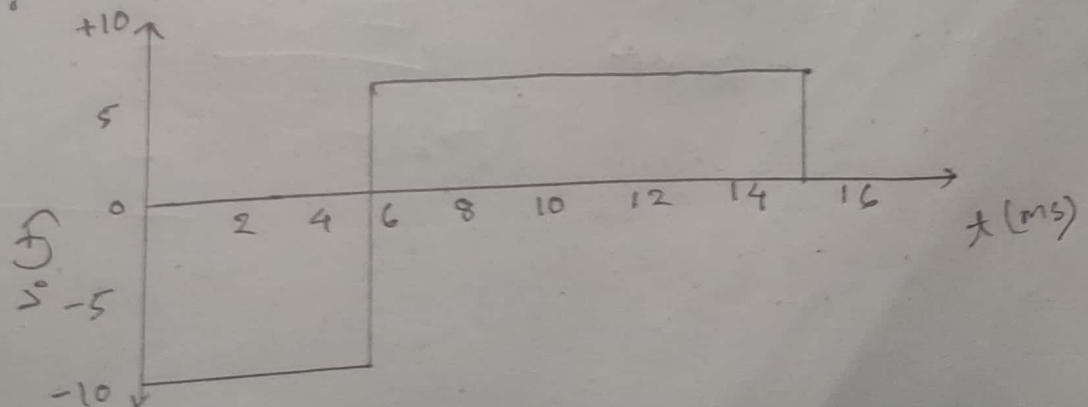

8

Ans to the Q.no:5

Given that,

$$R_f = 25 \text{ k}\Omega$$

$$R_i = 10 \text{ k}\Omega$$

$$V_i = 0.5 \text{ V}$$

a) We know that,

$$\begin{aligned} V_o &= \left(-\frac{25 \times 10^3}{10 \times 10^3} \right) \times 0.5 \\ &= -1.25 \text{ V} \quad (\text{Ans}) \end{aligned}$$

b) The current through the $10 \text{ k}\Omega$ resistor,

$$\begin{aligned} i &= \frac{V_i - 0}{R_i} \\ &= \frac{0.5 - 0}{10 \times 10^3} \\ &= 5 \times 10^{-5} \text{ A} \\ &= 50 \text{ }\mu\text{A} \quad (\text{Ans}) \end{aligned}$$