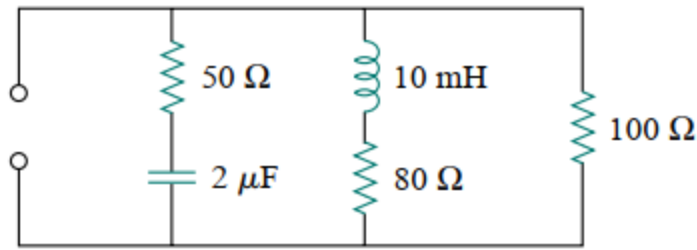


## Class Test \_2

Q.1. The network in the following figure is part of the schematic describing an industrial electronic sensing device. What is the total impedance of the circuit at 2 kHz?




Q.2. A power transmission system is modeled as shown in the following figure. Given the source voltage

$V_s = 115\ 0^\circ\ \text{V}$ , source impedance

$Z_s = 1 + j0.5$ , line impedance

$Z_l = 0.4 + j0.3$ , and load impedance

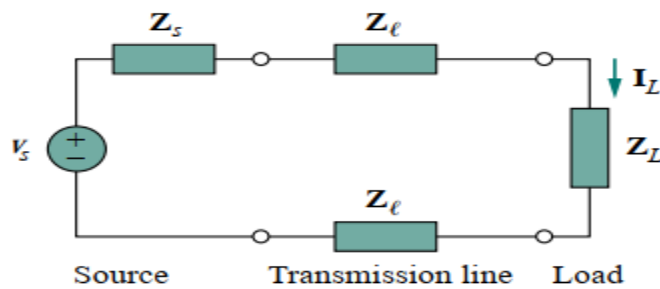$Z_L = 23.2 + j18.9$ , find the load current  $I_L$ .



Q.3. Compute the rms value of the waveform depicted in following figure.

