



# GREEN UNIVERSITY OF BANGLADESH



## Department of Computer Science & Engineering

Course Code: EEE-204

Course Title: Electronics lab

Experiment Number : 01

Experiment Name : Study of Diode I-V Characteristic

Date of Performance : 17.02.2021

Date of Submission : 05.04.2021

Submitted to:

Name : Sakib Abdul Ahad

Designation : Lecture

Dept. : EEE

Submitted by:

Name : Jakirul Islam

ID : 193002101

Dept. : CSE

Remark

Experiment no: 07

Experiment name: study of Diode I-v

characteristic.

Objectives:

1. To study the Diode I-v characteristics
2. To observe the output of a simple with a diode using AC input.

Instrument required:

serial	Name	Rating	Quantity
1	Project Board		1 piece
2	Diode		4 pieces
3	Resistor		1 piece
4	Multimeter		1 unit
5	Signal generator		1 piece
6	Oscilloscope		1 unit
7	Chords and wire		lot.

Circuit Diagram:

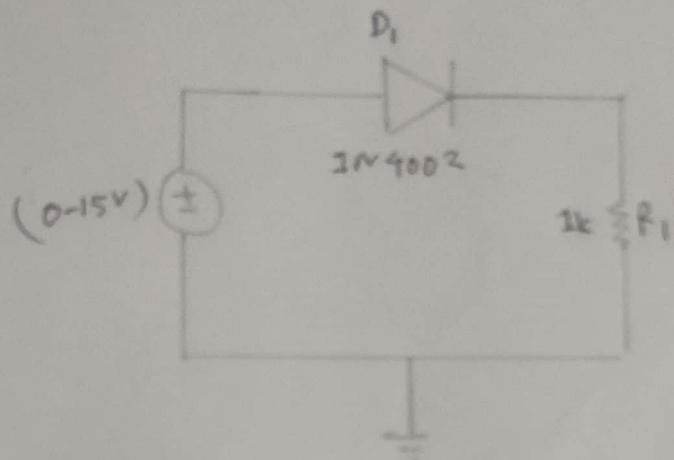


Fig: 2(a) : PN forward bias circuit

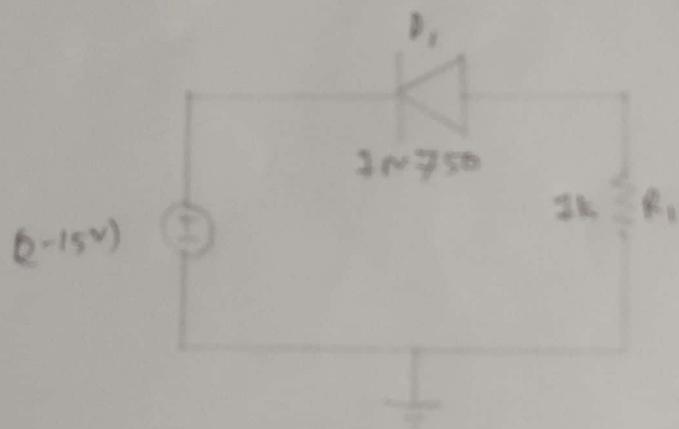


Fig: 2(b) : PN reverse bias circuit.

Description:-

A p-n junction diode is a two-terminal device that acts as a one way conductor. that means it permits the passage of electrical current in only one way and prevents if the current is passed from the other terminal. A diode can be connected in a circuit in two configurations.

1. forward Biased configuration
2. reverse Biased configuration

forward Bias, when the voltage at the p-side of a p-n diode is higher than that of its n-side. then the diode is called forward Biased.

reverse Bias, when a diode gets negative voltage across it then it is in reverse Biased

Breakdown voltage, when the voltage caused the burn is called breakdown voltage. There will be a rush of current at that time and that current is called Avalanche current


49

Experimental Data Table:

Serial	$V_{in}$ (v)	$V_o$ (v)	$I_o$ (mA)
1	0	0	0
2	0.2	0.57	0
3	0.5	0.60	0
4	0.7	0.61	0
5	1	0.62	0
6	1.2	0.63	0
7	1.5	0.65	5
8	1.7	0.66	7
9	2	0.68	10
10	2.2	0.688	12
11	2.5	0.696	15
12	2.7	0.699	16
13	3	0.703	17
14	3.2	0.709	18
15	3.5	0.715	20

5

Graph:

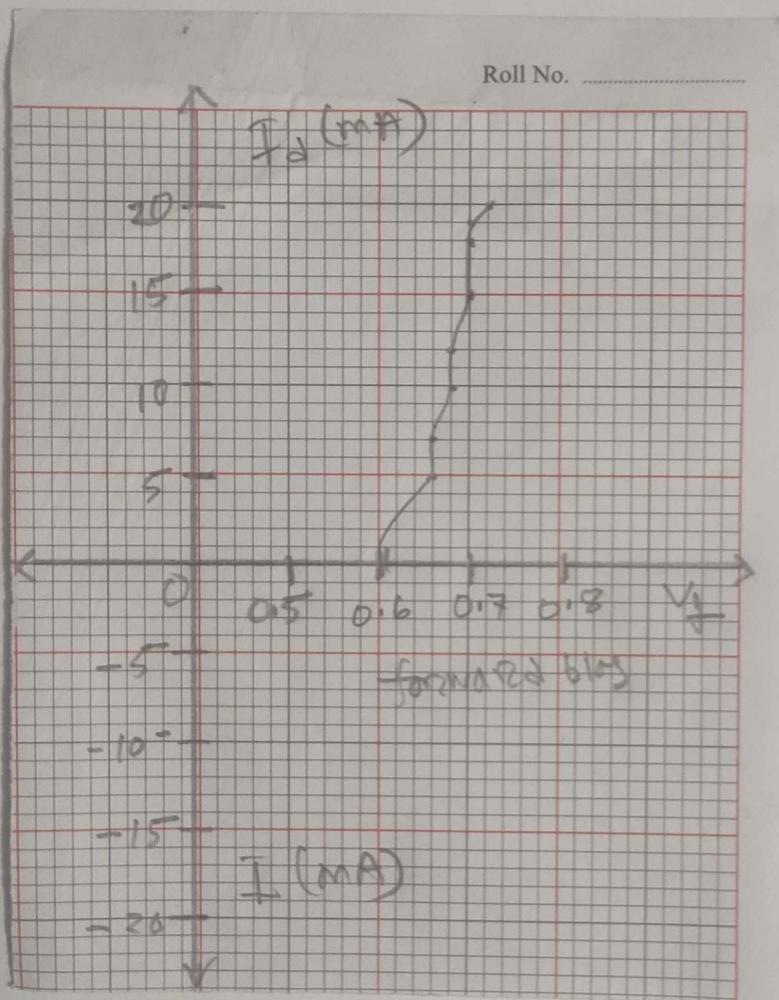

## Result:

## Discussions:

The diode should not be short circuited, that will allow the flow of huge current which might destroy the diode.

If we just reverse the diode to measure the I-v characteristics, the sudden change might destroy the diode.

Current must not pass through it for a very long time. It will then increase the depletion region and develop a fluctuating resistance.



# GREEN UNIVERSITY OF BANGLADESH



## Department of Computer Science & Engineering

Course Code: EEE-204

Course Title: Electronics lab

Experiment Number : 02

Experiment Name : Study of Diode Rectifier Circuits

Date of Performance : 23.02.2021

Date of Submission : 05.04.2021

Submitted to:

Name : Sakib Abdul Ahad

Designation : Lecture

Dept : EEE

Submitted by:

Name : Jakirul Islam

ID : 193002101

Dept : CSE

Remark


Objectives:

1. To understand Principle of diode in converting Ac into DC.
2. To study different diode rectifier circuits.


Instruments Required:

Serial	Name	Ratings	Quantity
1	Project Board		1 pieces
2	pn junction Diode		4 pieces
3	Resistor		1 piece
4	Zener Diode		1 piece
5	Capacitor		1 piece
6	Multimeter		1 unit
7	Signal Generator		1 piece
8	Oscilloscope		1 unit
9	Chords and wire		lot

Circuit diagram:

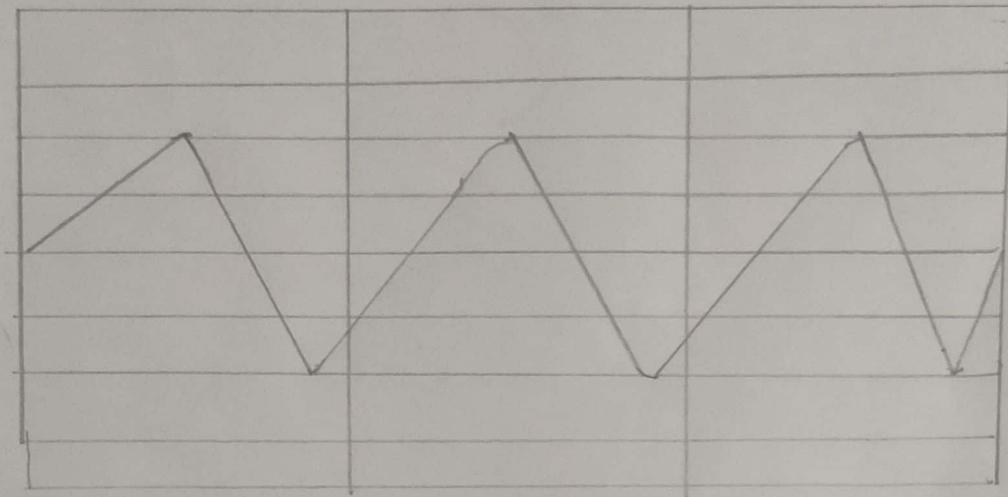

input voltage

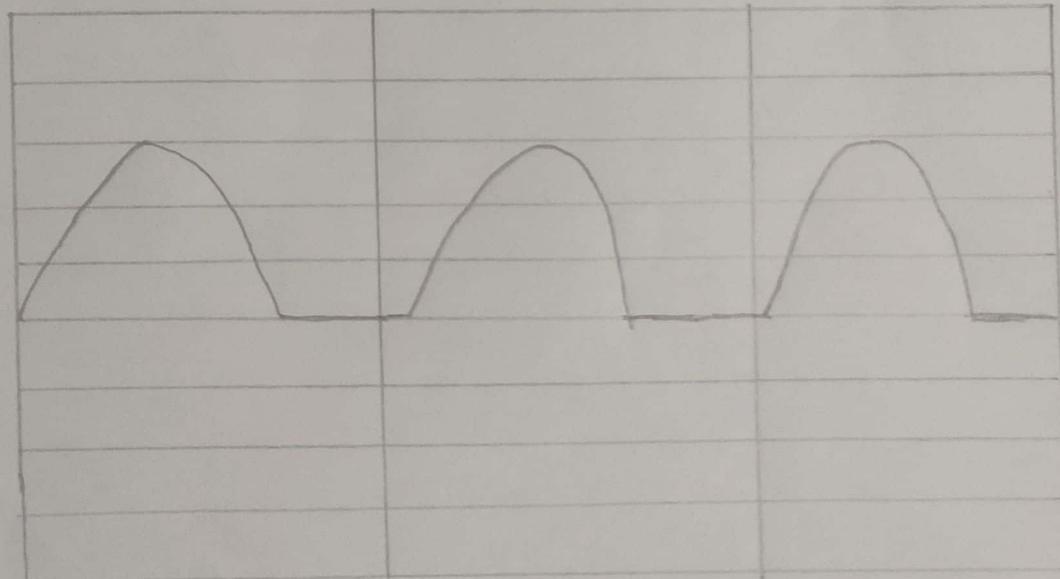

output voltage (without capacitor)

Figure 2.1: Half wave rectifiers Input and output

9

Circuit Diagram:

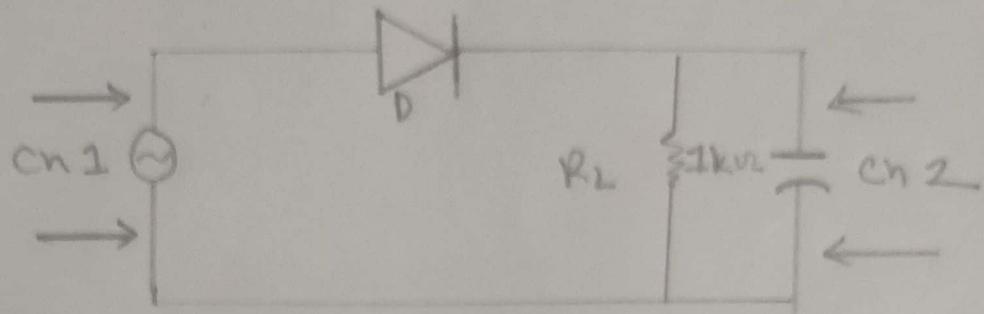


Figure: 2.3 Half wave rectifier

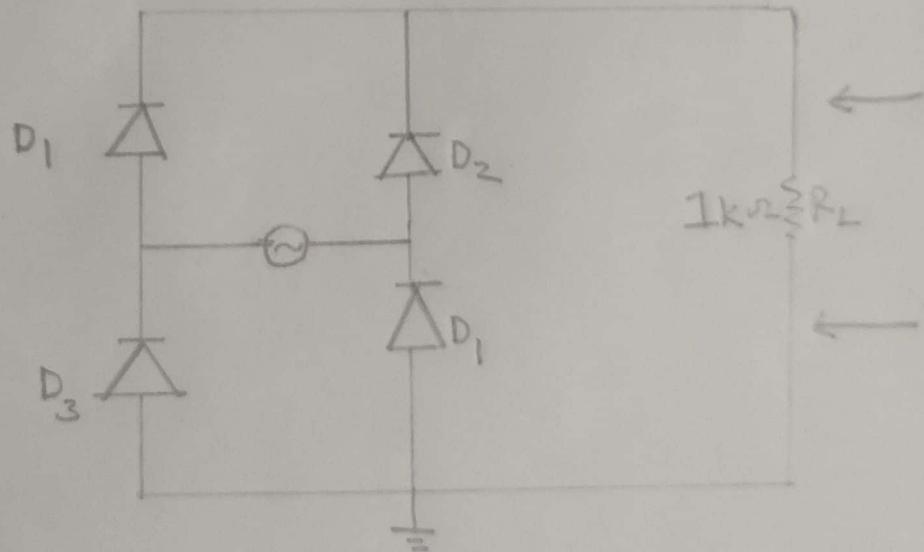


Figure: 2.4: Full wave rectifier

### Description:

In electrical systems AC to DC conversion is one of the most essential factors. The process of converting an AC voltage to DC voltage is called rectification.

There are two types of rectifiers

Half wave rectifier, which is a type of rectifier that allows only ~~one~~ one half cycle of an AC voltage waveform to pass while blocking the other half cycle.

Full wave rectifier, which is a type of rectifier that converts alternating current into continuous current and that utilizes both halves of each cycle of the alternating current.

### use of the capacitor:

The output voltage without the capacitor has not attained a DC shape. Instead it is an AC without its negative cycle. Now the way to achieve a DC voltage is to add a capacitor in parallel with lower resistance, before catching the next peak it will get discharged. So, a capacitor with higher capacitance is incumbent.


## Experimental Data and Table

Rectifier	output voltage	Theoretical value	Experiment value	
			without capacitor	
Half wave Rectifier	Average measured by multimeter DC node)			
Full wave rectifier	(average) measured by multimeter in D node			

table 2.1 output voltage measurement.


12

Graph:

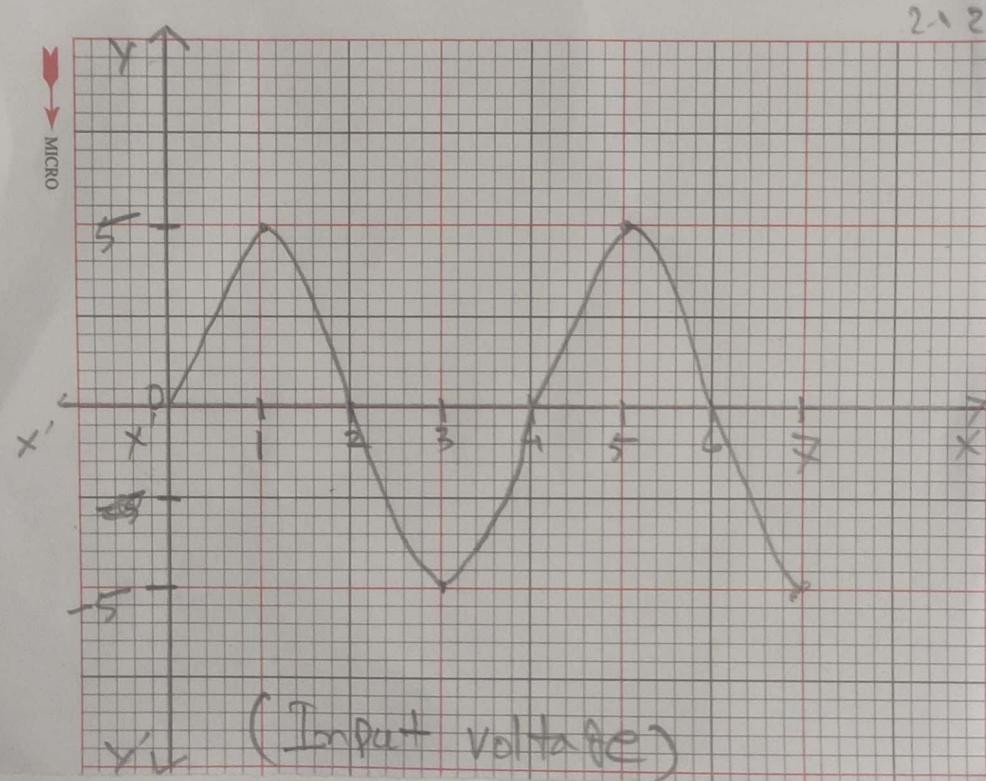

1?


Graph: 2.2

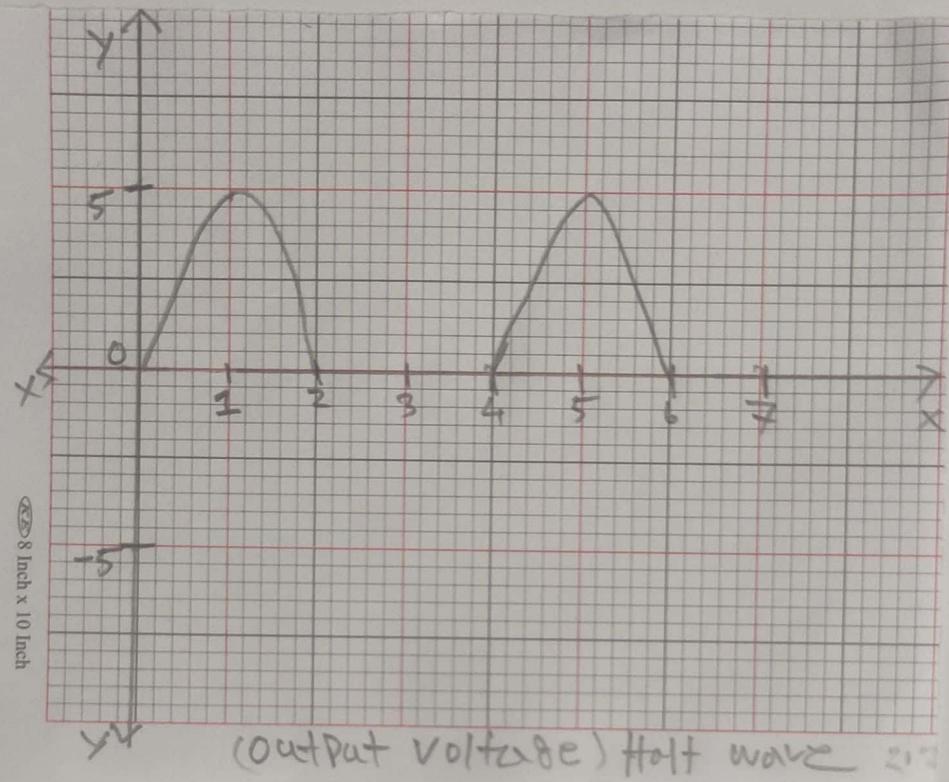

output voltage (Half wave rectifier)


14

Graph : 2.3

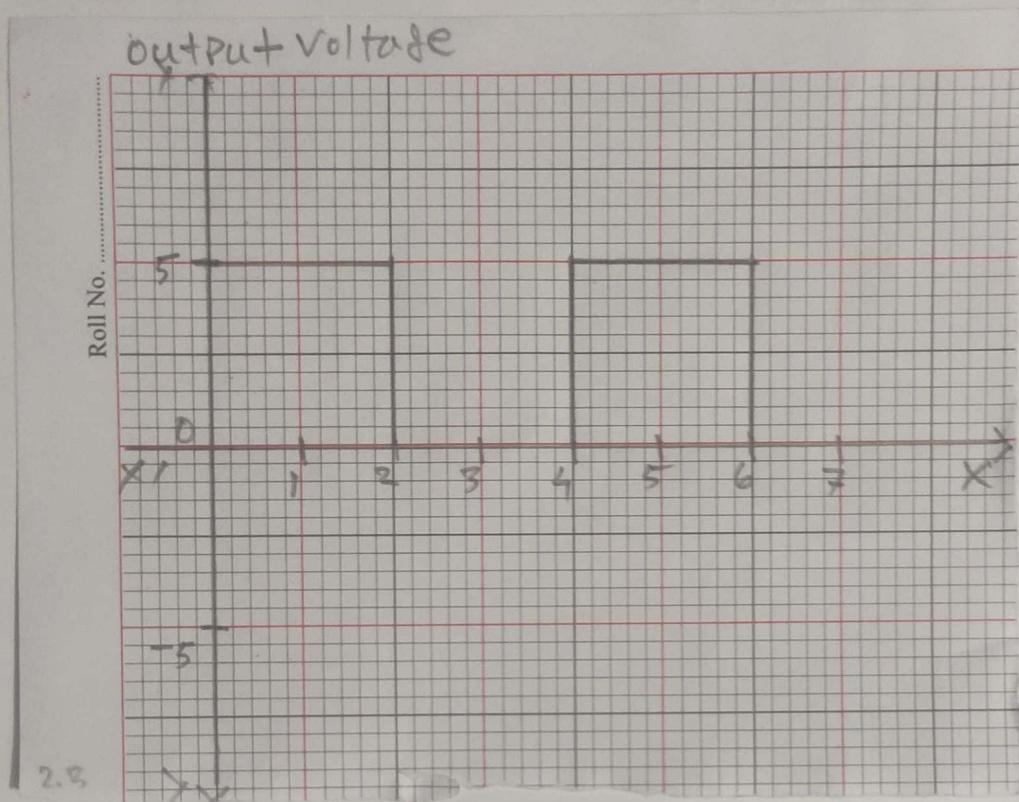

output voltage with capacitor  
(Half wave rectifier.)

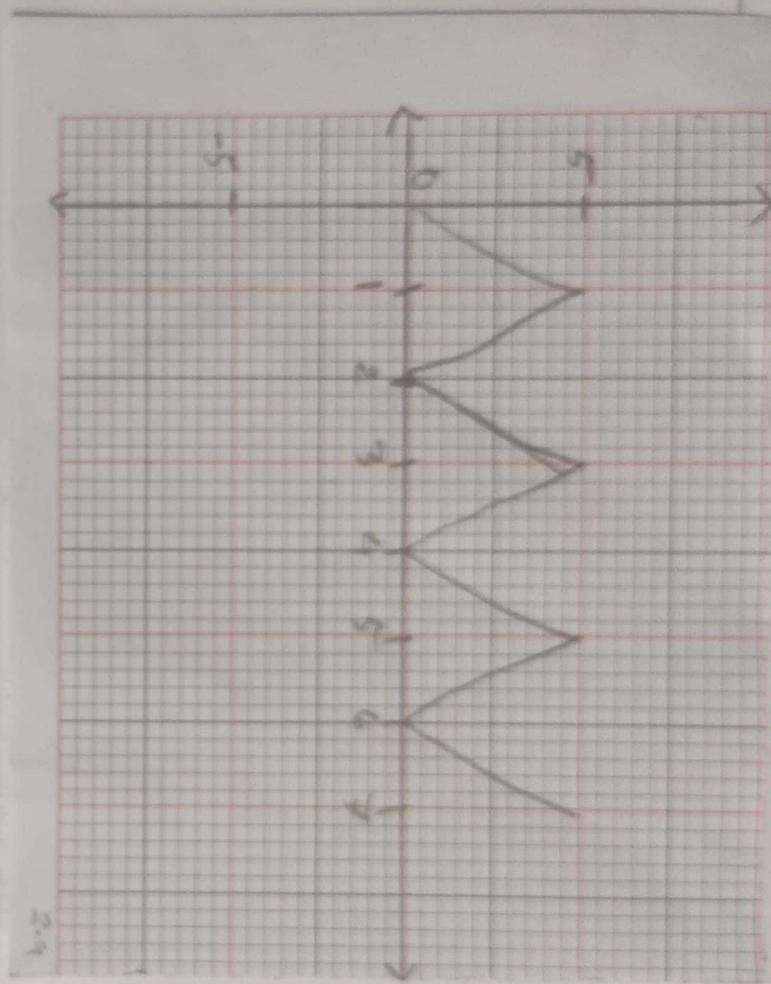Graph : 2.4 output voltage (Full wave rectifier)




15

158

calculation:

Graph: 2.5

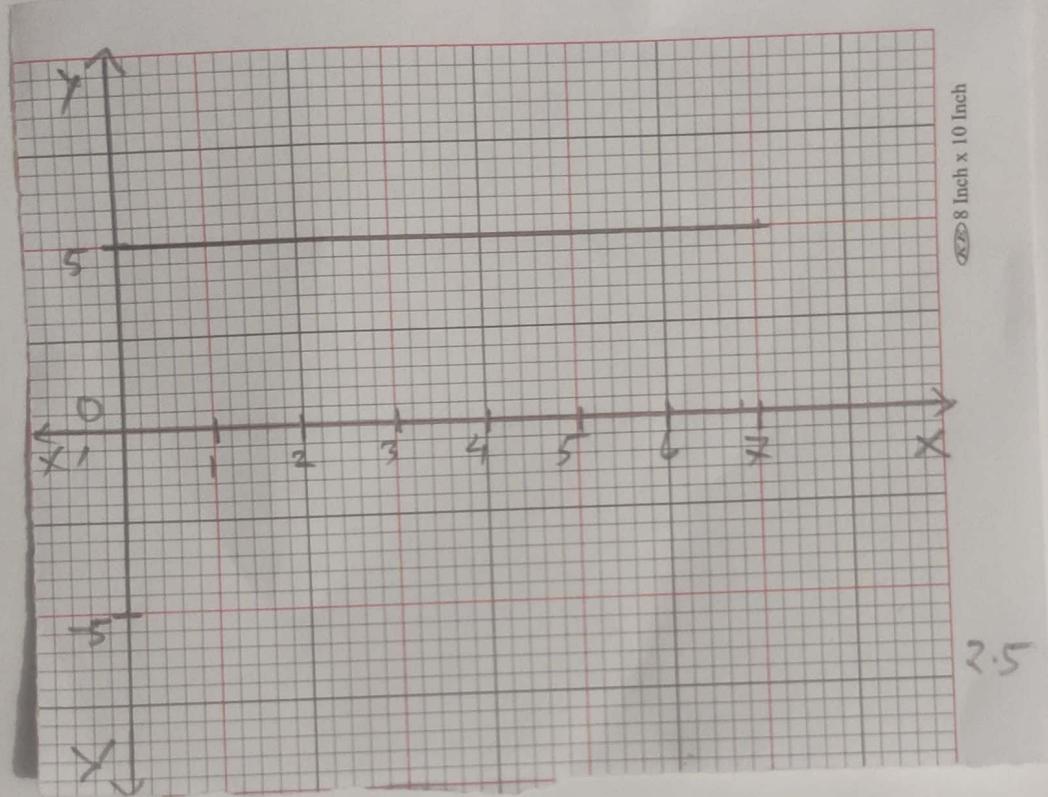

Graph: 2.5 output voltage with capacitor  
(full wave Rectifier)

Result:Discussion:

All the connections should be verified. The resistance should be chosen within the range of kohm. Best performance is being obtained within 50 Hz to 7 MHz.



# GREEN UNIVERSITY OF BANGLADESH



## Department of Computer Science & Engineering

Course Code: EEE-204

Course Title: Electronics lab

Experiment Number : 03

Experiment Name : Study of Operational Amplifier as Zero Crossing Samp;  
Voltage Level Detectors

Date of Performance : 02.03.2021

Date of Submission : 05.04.2021

**Submitted to:**

Name : Sakib Abdul Ahad

Designation : Lecture

Dept : EEE

**Submitted by:**

Name : Jakirul Islam

ID : 193002101

Dept : CSE

Remark

Objectives :

1. To get familiarized with Operational Amplifier
2. To study OP-AMP as a Comparator.

Instruments Required :

Serial	Name	Ratings	Quantity
1	Project Board		1 Piece
2	OP-AMP		1 Piece
3	Resistorz		7 Piece
4	Signal Generatorz		1 unit
5	Oscilloscope		1 unit
6	Analog Trainer Board		1 unit
7	Chords and wire		lot

Circuit Diagram:

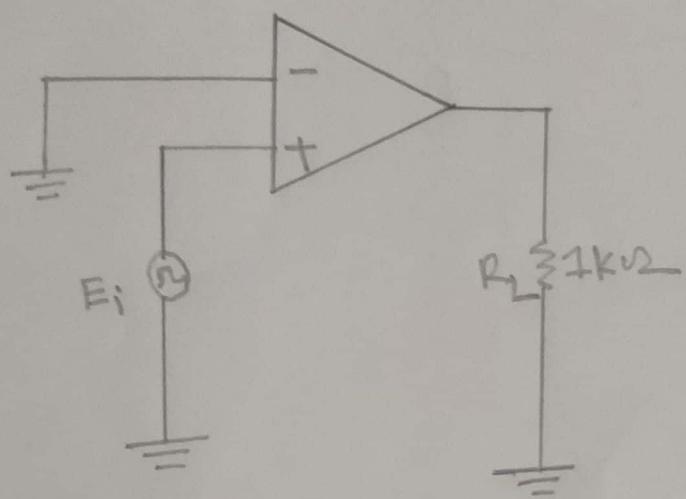


Figure : circuit diagram 1: non-inverting

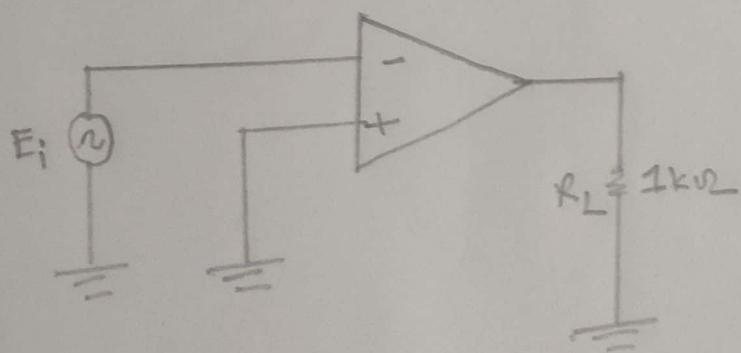


Figure : circuit diagram 2: inverting

### Description:

In open loop connection there is no feedback between the output and input terminal. The Op-Amp in this experiment will be operated as a comparator.


If the voltage of non-inverting input terminal is  $E^+$  and the voltage of the inverting input terminal is  $E^-$ , then,

the output,  $V_o = +V_{sat}$ , when  $E^+ > E^-$

And  $V_o = -V_{sat}$ , when  $E^+ < E^-$


Using this concept we can use it to detect any zero crossing voltage or to identify any voltage level.

Graph

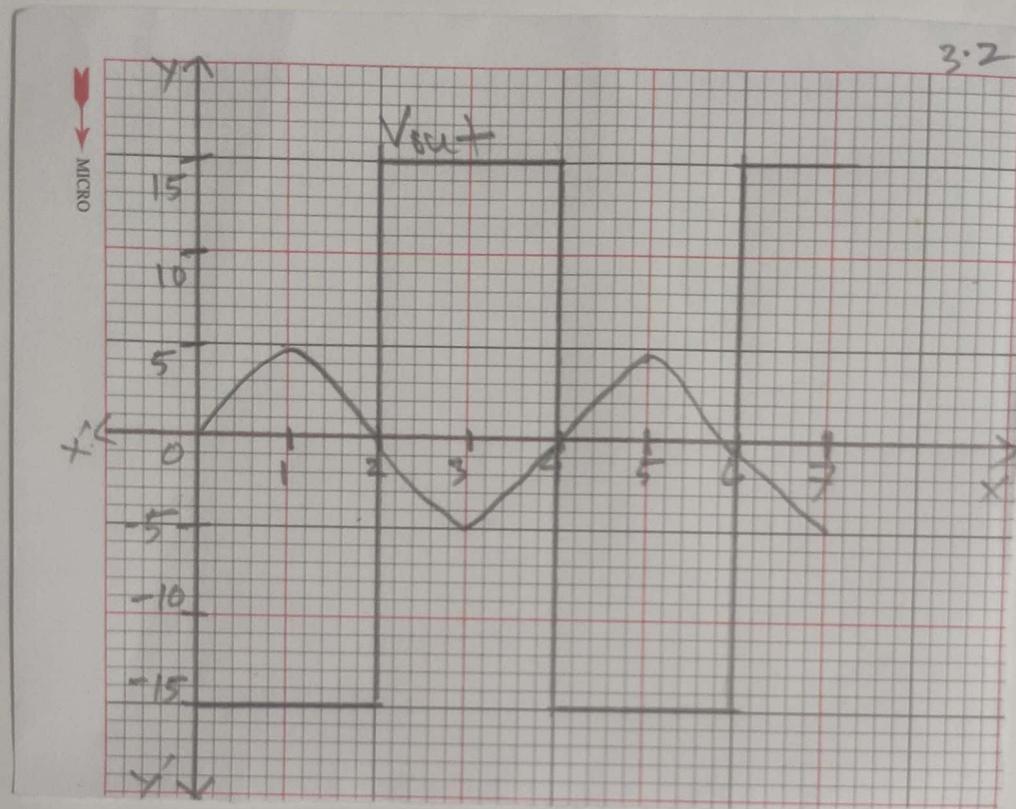

Graph 3.2:  $V_{in}$  and  $V_{out}$  for non-inverting zero crossing detector.

Graph:

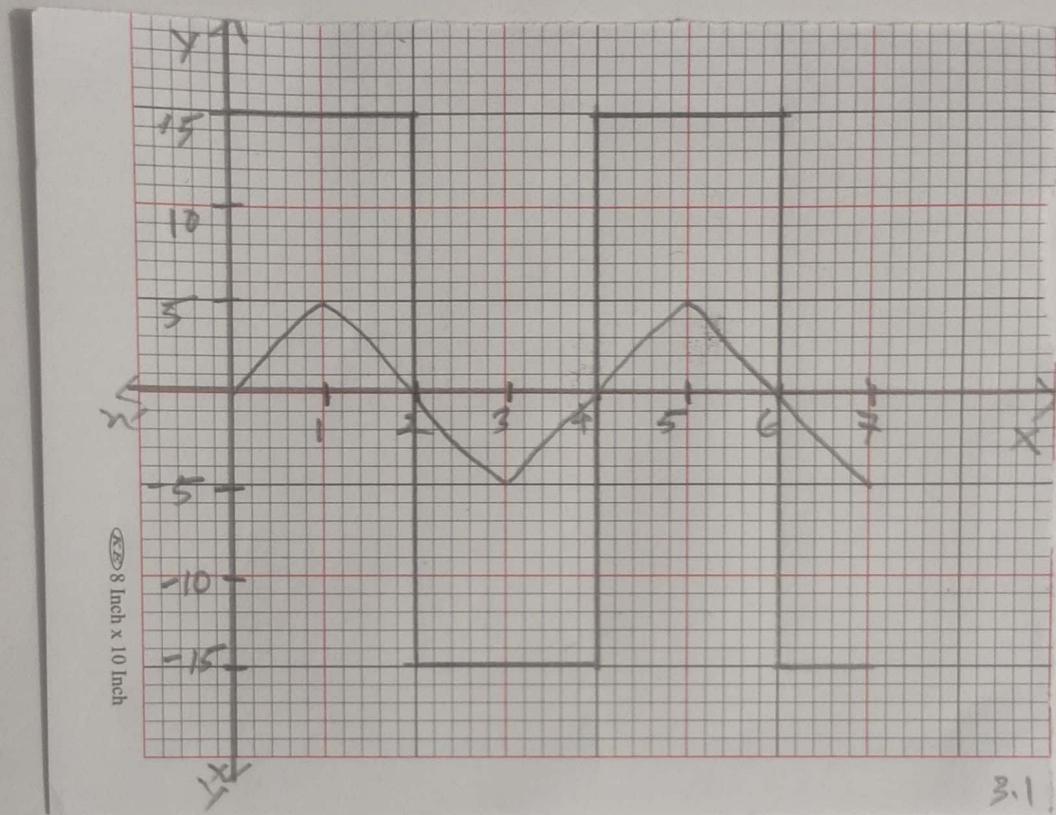

Graph 3.2:  $V_{in}$  and  $V_{out}$  for Inverting  
zero crossing detection.

### Discussion:

After completing this experiment  
we learn

1. After About the basic characteristics of an OP-Amp
2. We also understand the use of OP-Amp  
as a comparator.



## GREEN UNIVERSITY OF BANGLADESH



### Department of Computer Science & Engineering

Course Code: EEE-204

Course Title: Electronics lab

Experiment Number : 04

Experiment Name : Study of Operational Amplifier as an Amplifier

Date of Performance : 30.03.2021

Date of Submission : 05.04.2021

Submitted to:

Name : Sakib Abdul Ahad

Designation : Lecture

Dept. : EEE

Submitted by:

Name : Jakirul Islam

ID : 193002101

Dept. : CSE

Remark

### Objectives:

1. To get familiarized with the use of OPAMP as amplifiers.
2. To study the behaviour of inverting and non-inverting amplifiers.

### Instruments Required:

Serial	Name	Ratings	Quantity
1	Project Board		1 piece
2	OP-AMP		1 piece
3	resistor		1 piece
4	Signal Generator		1 unit
5	oscilloscope		1 unit
6	DC Power Supply		1 unit
7	Multimeter		1 unit
8	Chords and wire		lot

Circuit Diagram:

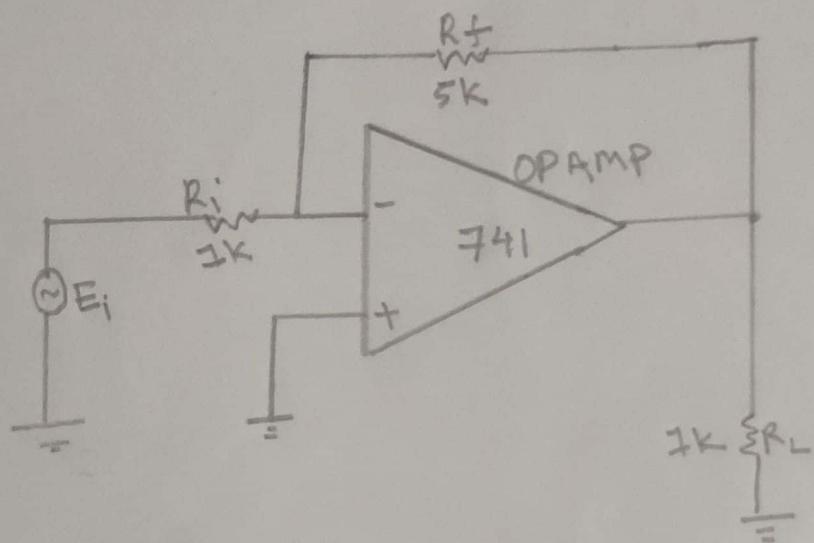


figure: Circuit Diagram 1

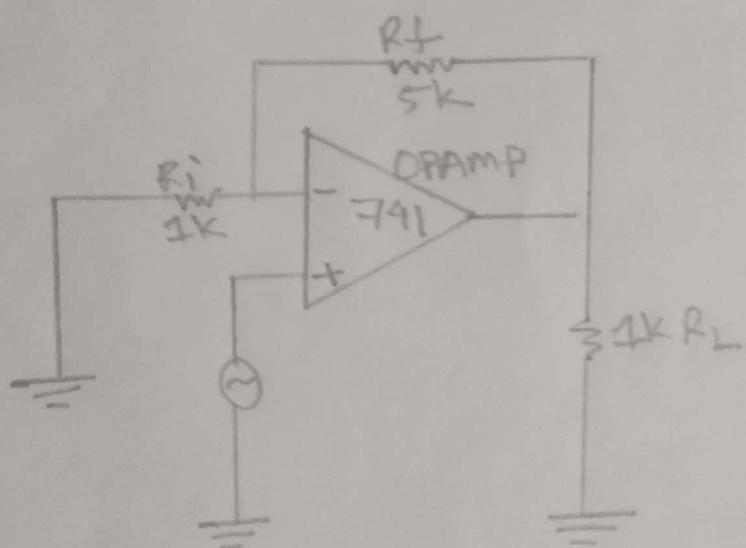


figure: Circuit Diagram 2

Description:

The two widely used closed loop amplifiers using OPAMP are -

1. Inverting Amplifier
2. Non-inverting Amplifier

In both the cases the closed loop gain of the Amplifiers is determined by the input resistance  $R_i$  and the feedback resistance  $R_f$ .

**Inverting Amplifier:** In an inverting amplifier the input is applied at the inverting input pin. The output obtained here is inverting. The close loop gain for this type of amplifier is given by

$$A_{cl} = -R_f / R_i$$

**Non-inverting Amplifier:** In this type of amplifier the input is applied at the non-inverting input whereas the output is not inverting. The close loop gain for this type of amplifier is given by

$$A_{cl} = (1 + R_f / R_i)$$

Experimental Data Table:


Table 4.1: Inverting Amplifier

$R_i$	$R_f$	$A_{CL} = -R_f/R_i$	$E_i$	$V_o$	$Gain = \frac{V_o}{E_i}$
1 k $\Omega$	2 k $\Omega$	-2	4 V	8 V	402


Table 4.2: Non-Inverting Amplifier

$R_i$	$R_f$	$A_{CL} = (1 + \frac{R_f}{R_i})$	$E_i$	$V_o$	$Gain = \frac{V_o}{E_i}$
1 k $\Omega$	2 k $\Omega$	3	2 V	6 V	3

Graph

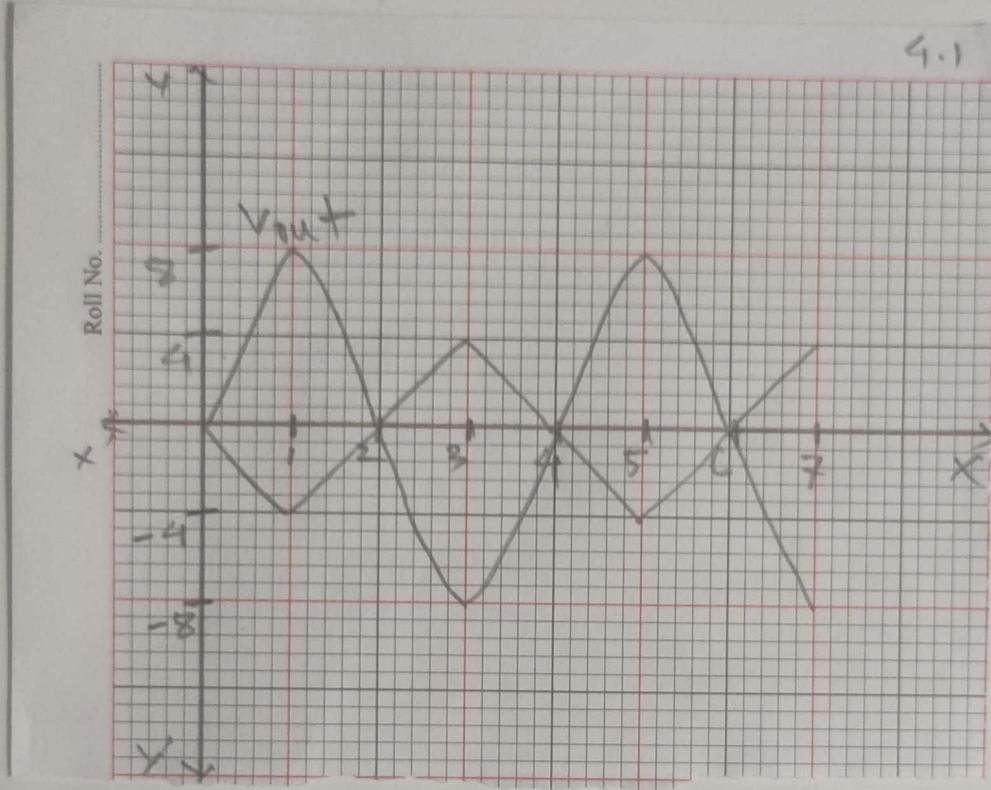

Graph

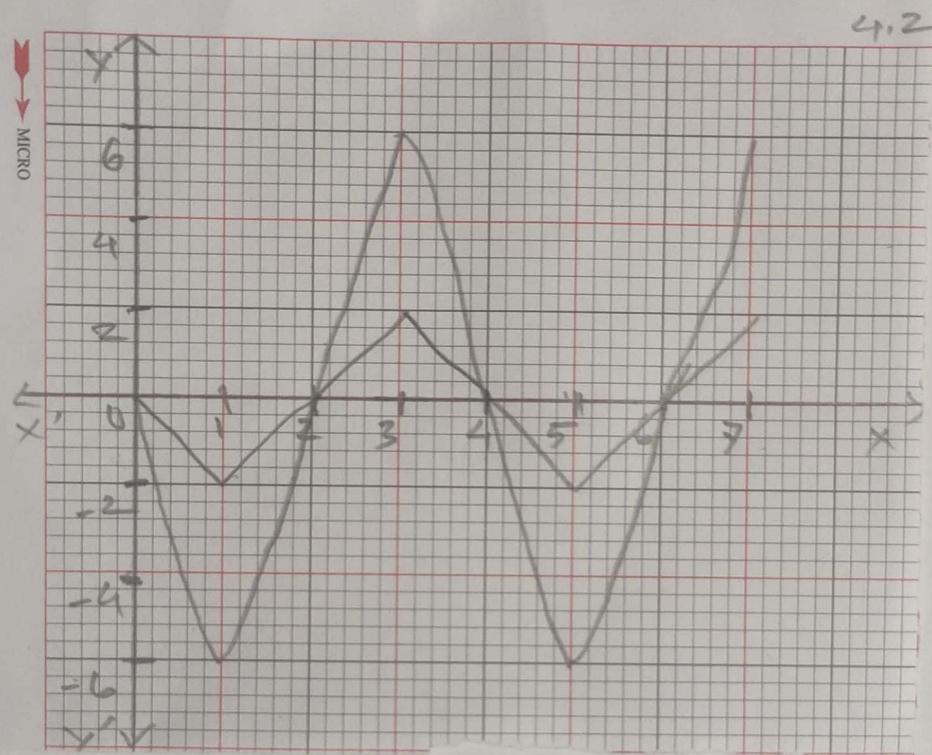

Graph: 4.2:  $V_{in}$  and  $V_{out}$  for non-inverting Amplifier

### Discussion:

After completing this experiment we learn-

- a) About the operational of op amp as an amplifier.
- b) we also point out the difference of behavior of the inverting and non-inverting amplifier.



**GREEN UNIVERSITY OF BANGLADESH**  
**Department of Computer Science & Engineering**

# **Lab report-9b**

**Course Code: EEE204**

**Course Title: Electronics Lab**

**Experiment name: Study of Mathematical Operations Using Op Amp**

**Submitted to:**

Name : Sakib Abdul Ahad

Designation : Lecture

Dept : CSE

Green University Of Bangladesh

**Submitted by:**

Name : Jakirul islam

ID : 193002101

Section : 193

Dept. : CSE

### Objective:

1. To study the use of operational Amplifiers in different mathematical operations.
2. To study the behavior of inverting adder, differentiator and integrator.

### Instrument Required:

Serial	Name	Ratings	Quantity
1	Project Board		1 Piece
2	OP-AMP	741	1 Piece
3	Resistor	10k $\Omega$	4 Piece
4	Resistor	20k $\Omega$ , 50k $\Omega$	1 Piece
5	Capacitor	0.01 $\mu$ F	1 piece
6	Signal Generator		1 unit
7	Oscilloscope		1 unit
8	DC Power Supply		1 unit
9	Multimeter		1 unit
10	Chords and wire		lot

Circuit Diagram:

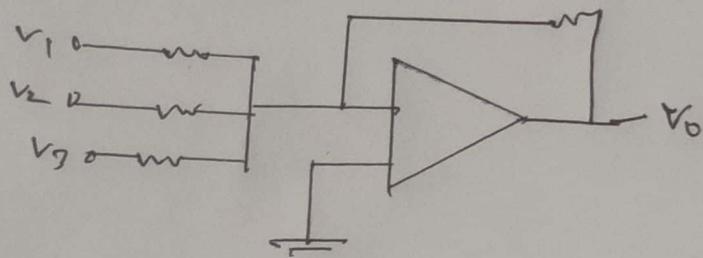


Fig: 5.1 Inverting adder

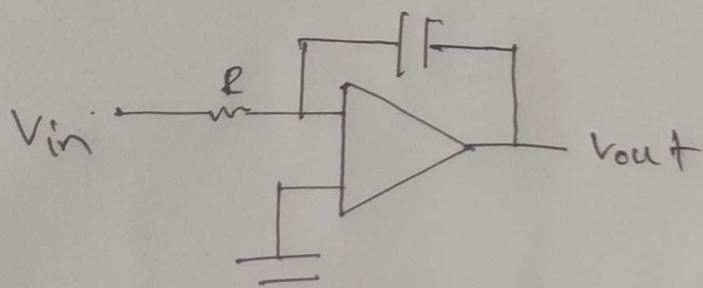


Fig: 5.2 Integrator

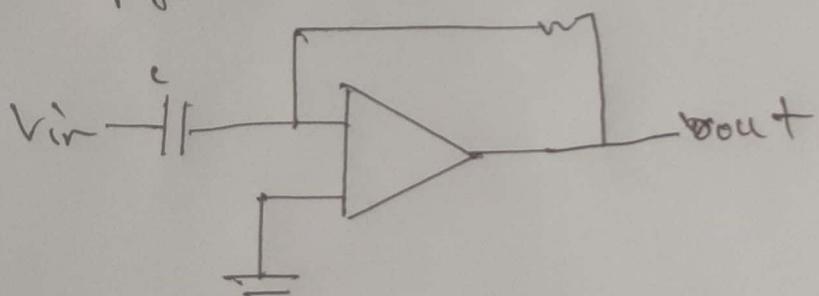


Figure: 5.3 Differentiator

Description:

The property of infinite impedance and infinite gain of an operational amplifier results in a situation of zero voltage between the two input terminals. Due to this effect, the OP-Amp can be used to perform some mathematical operations like OP-amps in different mathematical operations. Implement OP-Amp circuits in diverse systems to serve different purposes. Using the concept of inverting amplifier, the OP-Amp can be used as an adder (actually inverting adder to sum up same input signals).

Discussion :

After completing this experiment we learn-

- a) About the use of op-Amp in different mathematical operations.
- b) we also learn about the Implementation of op-Amp Circuits in diverse systems to serve different purpose.